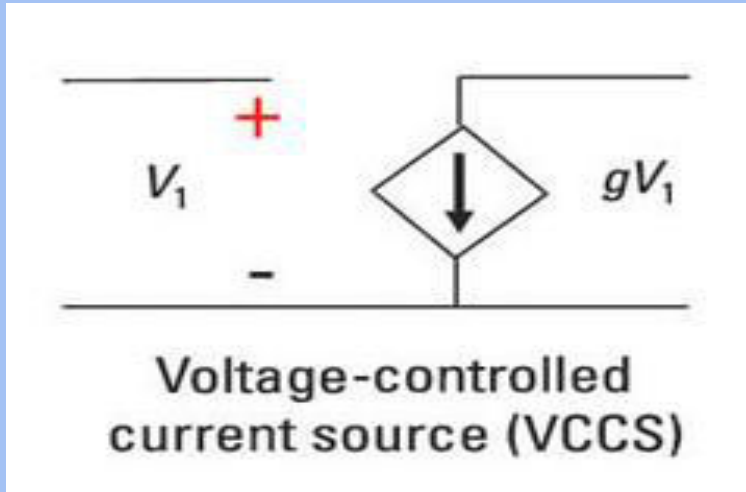


# **Voltage-Controlled Current Source**

**Elementrix Classes**

# Voltage-Controlled Current Source

With a voltage across the input, you can control the amount of current output.



The VCCS dependent source has a proportionality constant  $g$ , called the **transconductance** (ratio of the change in the output current to the change in the input voltage).

## Example:

Let's assume some values for the components:

**Input Voltage ( $V_{in}$ ):** 10 volts

**Transconductance ( $g$ ):** 0.002 Siemens (2 mS)

## Calculations:

Using the formula for the VCCS:

$$I_{out} = g \cdot V_c$$

Substitute the given values:

$$I_{\text{out}} = (0.002\text{S}) \cdot (10\text{V})$$

$$I_{\text{out}} = 0.02\text{A}$$

**Therefore, with an input voltage of 10 volts and a VCCS transconductance (g) of 0.002 Siemens, the output current ( $I_{\text{out}}$ ) would be 0.02 amperes in this example.**

**This example demonstrates how a Voltage-Controlled Current Source can generate an output current that is proportional to a controlling voltage. The transconductance (g) represents the proportionality constant in this context.**

पढ़िए और पढ़ाइये

**SUBSCRIBE, SHARE, COMMENT**