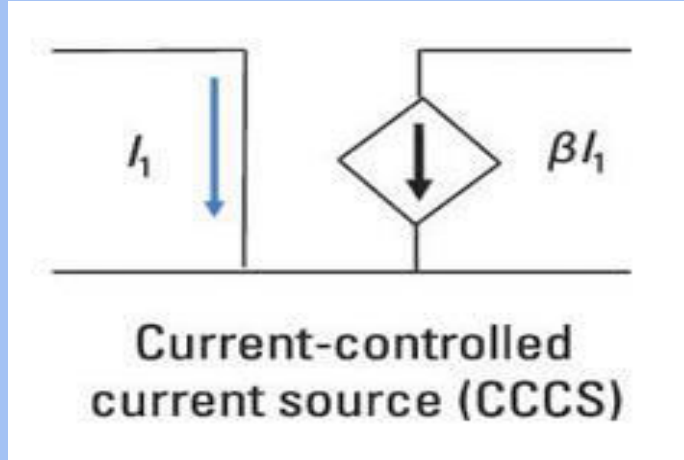


# Current-Controlled Current Source

Elementrix Classes

# Current-Controlled Current Source

With a current flowing through the input port, you can control a dependent current source at the output port.



For the CCCS dependent source, you can think of the proportionality constant  $\beta$  as the current gain because it's the **ratio of current output to current input**.

## Example:

Let's assume some values for the components:

**Controlling Current ( $I_c$ ):** 2 milliamperes (2 mA)

**Current Gain ( $\beta$ ):** 3 (unitless)

## Calculation:

Using the formula for the CCCS:

$$I_{\text{out}} = \beta \cdot I_c$$

Substitute the given values:

$$I_{\text{out}} = (3) \cdot (2\text{mA})$$

$$I_{\text{out}} = 6\text{mA}$$

**Therefore, with a controlling current of 2 mA and a CCCS current gain ( $\beta$ ) of 3, the output current ( $I_{\text{out}}$ ) would be 6 mA in this example.**

**This example illustrates how a Current-Controlled Current Source can generate an output current that is proportional to a controlling current. The current gain ( $\beta$ ) represents the proportionality constant in this context.**

पढ़िए और पढ़ाइये

**SUBSCRIBE, SHARE, COMMENT**