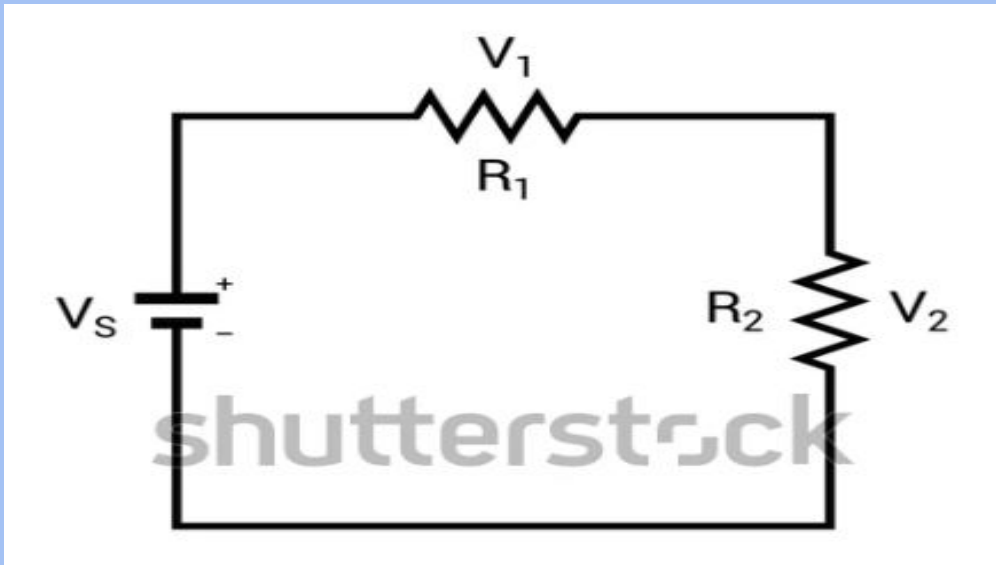


Voltage Divider Rule

Elementrix Classes

Voltage Divider Rule

Let's consider a simple series circuit with two resistors, R_1 and R_2 , connected in series, and a voltage source (V_{total}) connected across the combination.



1. Define the Voltages and Resistances:

$$V_{\text{total}} = 10 \text{ volts}$$

$$R_1 = 3\Omega$$

$$R_2 = 5\Omega$$

2. Calculate Total Resistance (R_{total}):

$$R_{\text{total}} = R_1 + R_2 = 3 + 5 = 8\Omega$$

3. Apply Voltage Divider Rule for R_1 :

$$V_1 = V_{\text{total}} \times \frac{R_1}{R_{\text{total}}} = 10 \times \frac{3}{8} = \frac{30}{8} = 3.75 \text{ volts}$$

$$\mathbf{V_1 = 3.75 \text{ volts}}$$

4. Apply Voltage Divider Rule for R_2 :

$$V_2 = V_{total} \times \frac{R_2}{R_{total}} = 10 \times \frac{5}{8} = \frac{50}{8} = 6.25 \text{ volts}$$

$$V_2 = 6.25 \text{ volts}$$

This means that in the given series circuit, 3.75 volts is dropped across the 3-ohm resistor (R_1), and 6.25 volts is dropped across the 5-ohm resistor (R_2). **The sum of these individual voltages equals the total voltage (V_{total}), confirming the conservation of energy in the circuit.**

पढ़िए और पढ़ाइये

SUBSCRIBE, SHARE, COMMENT