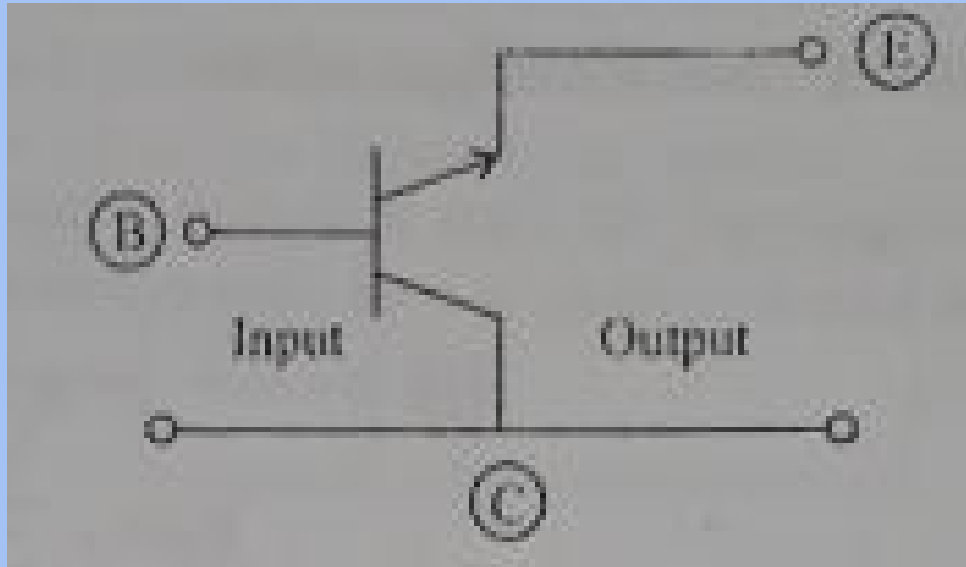


Common Collector Configuration of Transistor

Elementrix Classes

Common Collector Configuration of Transistor

In this configuration, collector is common to input and output circuit.



Current amplification factor (γ): It is defined as the ratio of change in emitter current to the change in base current at constant collector emitter voltage V_{CE} .

$$\gamma_{dc} = \left. \frac{\Delta I_E}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

If only dc values are considered,

$$\gamma_{dc} = \frac{I_E}{I_B}$$

पढ़िए और पढ़ाइये

SUBSCRIBE, SHARE, COMMENT