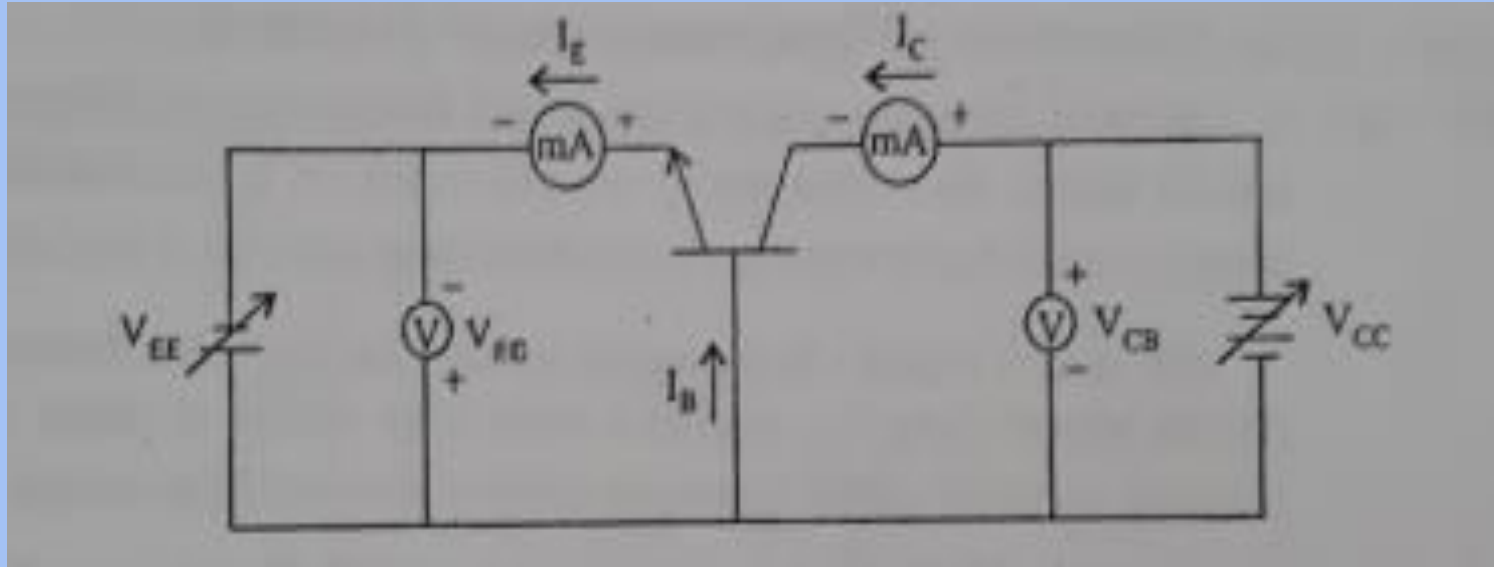


# **Common Base Configuration of Transistor Input/Output Characteristics**

Elementrix Classes

# Common Base Configuration Characteristics




# Input Characteristics
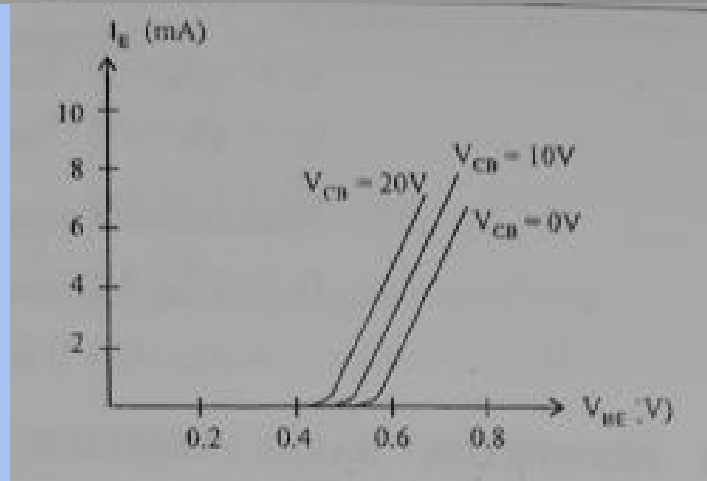
## Input characteristics

It is the graph of input current  $I_E$  versus input voltage  $V_{BE}$  when output voltage  $V_{CB}$  is kept constant.

For a given  $V_{CB}$ , the input characteristic resembles the characteristic of forward biased diode. Input current  $I_E$  increases as input voltage  $V_{BE}$  increases for fixed value of  $V_{CB}$ . For a given value of  $V_{BE}$ ,  $I_E$  increases with increase in  $V_{CB}$  due to early effect.



As  $V_{CB}$  increases, width of the depletion layer in the base increases. Hence the width of the base available for conduction decreases. The reduction in the width of the base due to increase in reverse bias is known as early effect. Due to early effect, the chances of recombination of electrons with the holes in the base decreases. Therefore, base current decreases but more electrons can travel from emitter to collector terminal. Therefore, collector current increases with increase in emitter current  $I_E$ .

As reverse bias voltage  $V_{CB}$  further increases, at one stage the depletion region completely occupies the base at which collector base junction breaks down. This phenomenon is known as punch-through.

Dynamic input resistance  $r_i = \left. \frac{\Delta V_{BE}}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$


# Output Characteristics

## Output characteristics

It is the graph of output current  $I_C$  versus output voltage  $V_{CB}$  for given values of  $I_E$ .

There are three different regions in output characteristics :

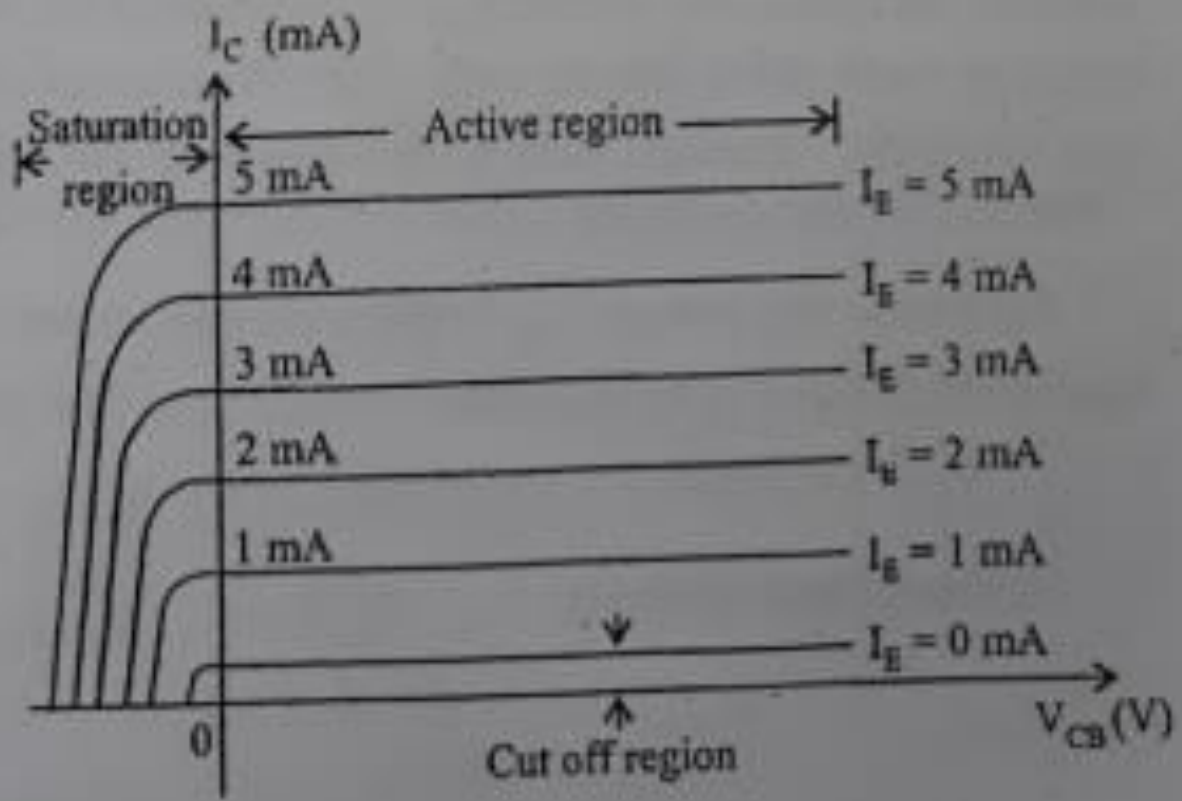- (i) **Cut-off region** : In this region, both the junctions are reverse biased. When emitter-base junction is reverse biased, the current due to majority carrier i.e.  $I_E$  is zero. Since collector-base junction is reverse biased, current due to minority carriers flows from collector to base which is represented as  $I_{CBO}$ .
- (ii) **Active region** : In this region, emitter-base junction is forward biased and collector base junction is reverse biased. Once  $V_{CB}$  reaches a value large enough to ensure a large portion of electrons enter the collector, collector current  $I_C$  remains constant as shown by horizontal lines. As  $I_E$  increases,  $I_C$  increases.
- (iii) **Saturation region** : In this region, both the junctions are forward biased. When  $V_{CB}$  is negative, collector base junction is actually forward biased. Thus the graphs are drawn on negative side of  $V_{CB}$ . In this region, there is large change in collector current with small increase in voltage  $V_{CB}$ .



Output resistance

$$r_o = \left. \frac{\Delta V_{CB}}{\Delta I_C} \right|_{I_E = \text{constant}}$$

Current gain

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$$

पढ़िए और पढ़ाइये

**SUBSCRIBE, SHARE, COMMENT**