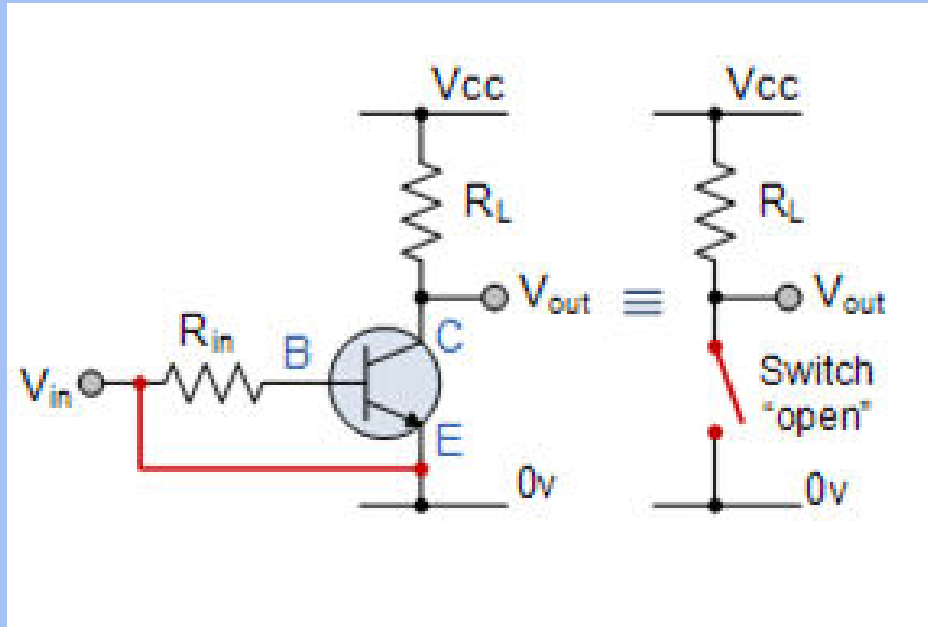


Transistor as a Switch

Elementrix Classes


Transistor as a Switch

❑ Cut-off Region




- The input and Base are grounded (0v)
- Base-Emitter voltage $V_{BE} < 0.7v$
- Base-Emitter junction is reverse biased
- Base-Collector junction is reverse biased
- Transistor is “fully-OFF” (Cut-off region)
- No Collector current flows ($I_C = 0$)
- $V_{OUT} = V_{CE} = V_{CC} = “1”$
- Transistor operates as an “open switch”

□ Saturation Region

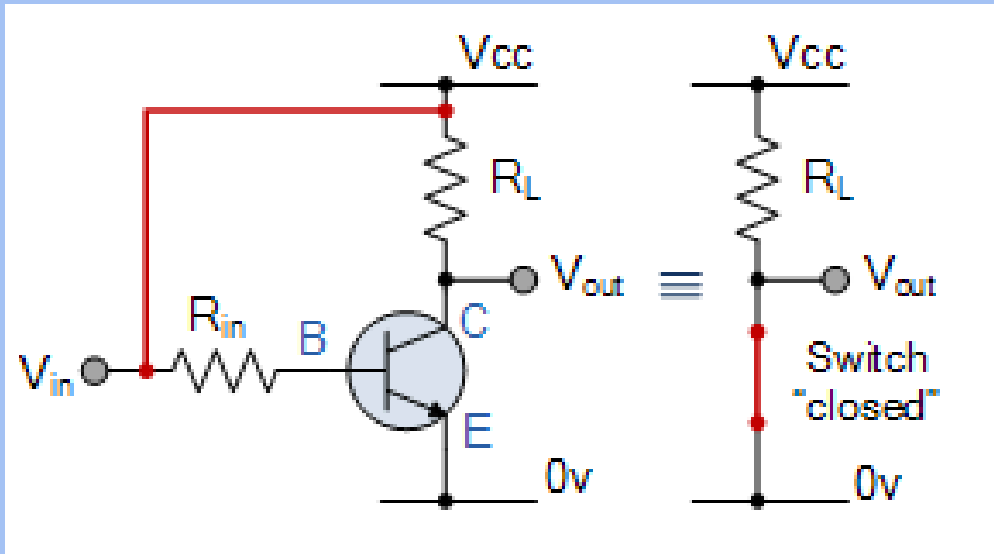

- The input and Base are connected to V_{CC}
- Base-Emitter voltage $V_{BE} > 0.7v$
- Base-Emitter junction is forward biased
- Base-Collector junction is forward biased
- Transistor is “fully-ON” (saturation region)
- Max Collector current flows ($I_C = V_{CC}/R_L$)
- $V_{CE} = 0$ (ideal saturation)
- $V_{OUT} = V_{CE} = “0”$
- Transistor operates as a “closed switch”

Operating Regions

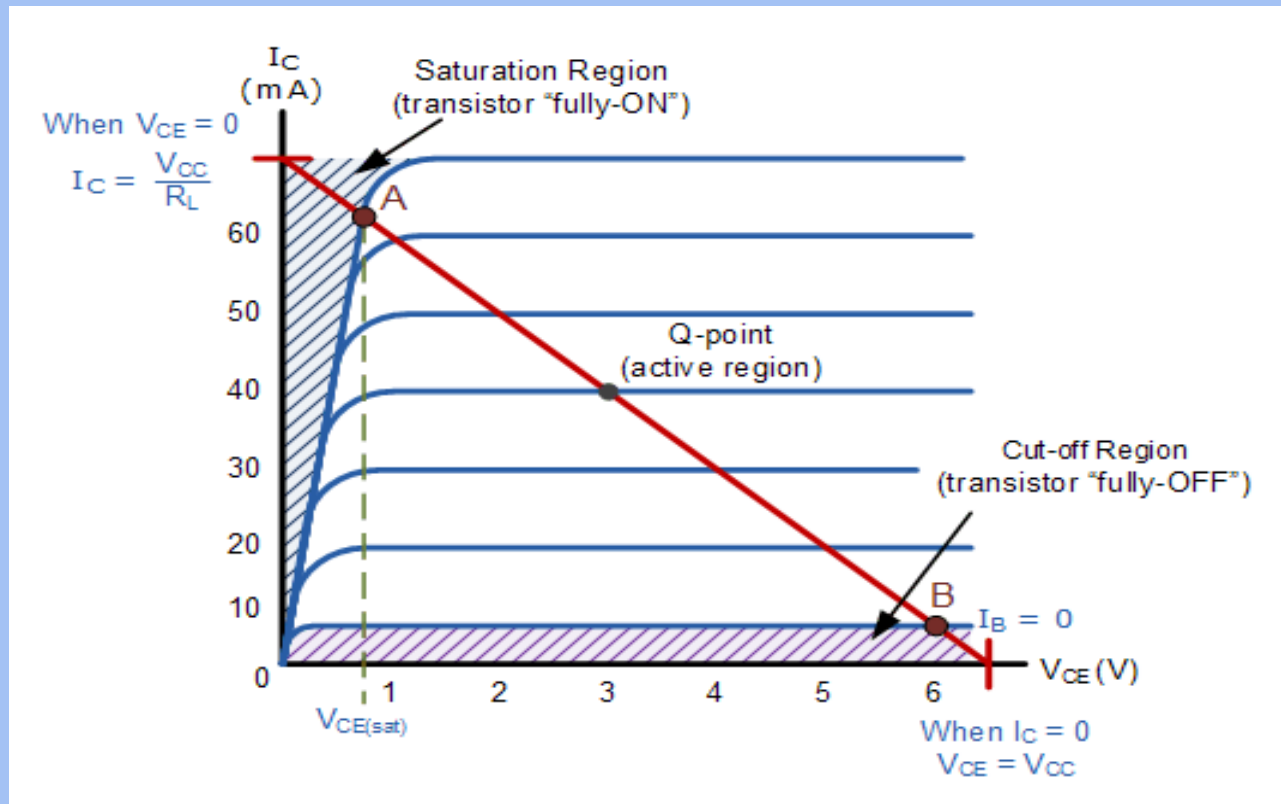

पढ़िए और पढ़ाइये

SUBSCRIBE, SHARE, COMMENT